



Figure 1 This circuit adds foldback-overcurrent protection to a linear regulator.