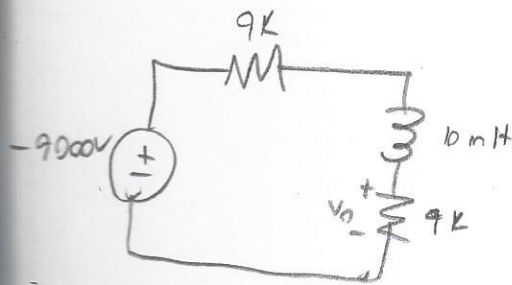


b) Using whatever method you like (yes, anything, don't raise your hand to ask if you can use XXX), provide a symbolic expression for the voltage $V_o(t)$ for $t > 0$ in the **BOX BELOW**. (17.5 points)

$$V_o(t) = i_L(t) R_3$$



$$V_L = L \frac{di}{dt}$$

$$V_L(t)$$

$$\tau = \frac{L}{R_{eq}} = \frac{10 \times 10^{-3}}{15,000}$$

$$i_L(t) = i_{\infty} + [i_{0^+} - i_{\infty}] e^{-t/\tau}$$

$$-0.5 + [-0.5 + 1] e^{-t/\tau}$$

$$-0.5 - 0.5 e^{-1.8 \times 10^{-6} t}$$

$$V_o(t) = 9000 [-0.5 - 0.5 e^{-1.8 \times 10^{-6} t}]$$

$$= -4500 - 4500 e^{-1.8 \times 10^{-6} t}$$

$$i_{L,0^+} = 1A$$

$$i_{L,\infty} =$$

$$t < 0 \quad V_L = L \frac{di}{dt}$$

$$i_{L,0^-} = -1A$$

$$i_{L,0^+} = i_{L,0^-} = -1A$$

$$i_{L,\infty} = -0.5A$$

