

Determine the minimum and the maximum loads currents for which the zener diode on figure below will maintain regulation. What is the minimum R_L that can be used?

$$V_z = 12V, I_{zK} = 3mA \text{ and } I_{zM} = 90mA$$

