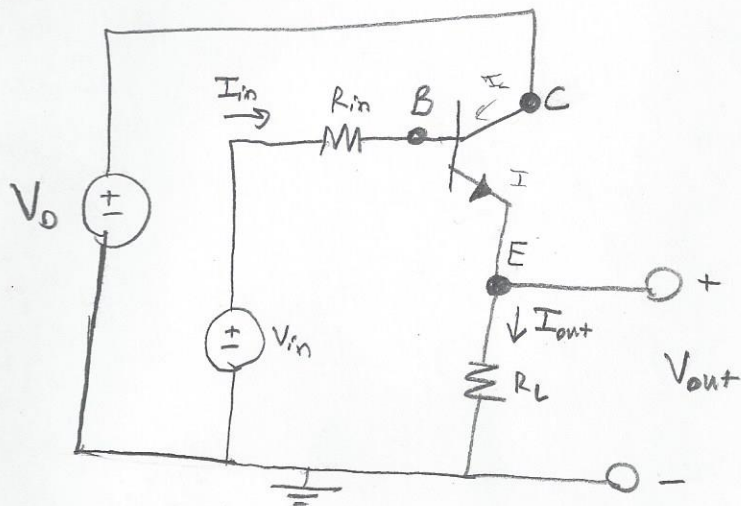



7



$$A_V = \frac{V_{out}}{V_{in}}$$

$$A_I = \frac{I_{out}}{I_{in}}$$

$$V_{in} \gg V_{BE}$$

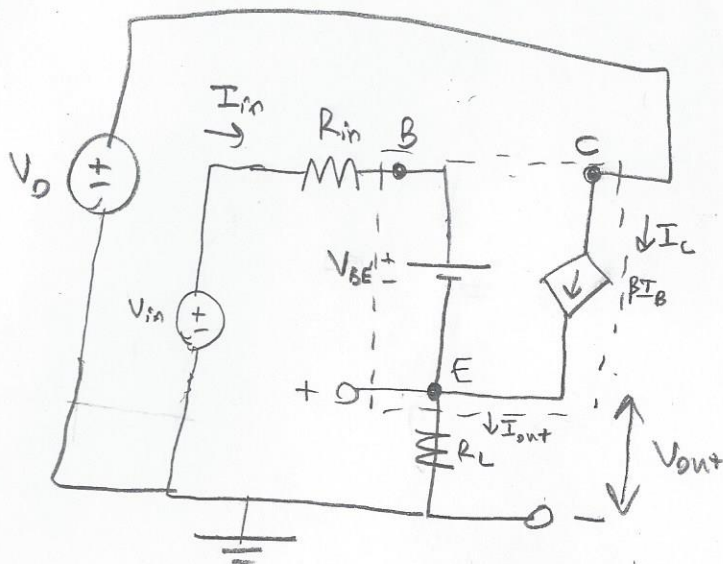

$$I_{out} = \beta I_{in}$$

$$A_I = \frac{\beta I_{in}}{I_{in}} = \beta$$

$$\frac{V_{in} - V_{BE}}{R_{in}} = I_{in}$$

$$I_{in} = \frac{V_{in}}{R_{in}}$$

$$V_{out} = \beta I_{in} R_L$$

$$A_V = \frac{\beta I_{in} R_L}{V_{in}}$$

$$A_V = \frac{\beta I_{in} R_L}{I_{in} R_{in}}$$

$$A_V = \frac{\beta R_L}{R_{in}}$$

$$A_I = \beta$$