

	$20\log(A)$	$20\log(1+j\omega RC)$	$20\log(1/ 1+j\omega R_3C)$	Sum of plots
1	-20.8	0.0	0.0	-20.8
10	-20.8	0.0	0.0	-20.8
100	-20.8	0.2	0.0	-20.7
1000	-20.8	1.7	-0.4	-19.5
10000	-20.8	7.6	-3.1	-16.4
100000	-20.8	16.8	-14.4	-18.5
1000000	-20.8	26.7	-32.8	-26.9

