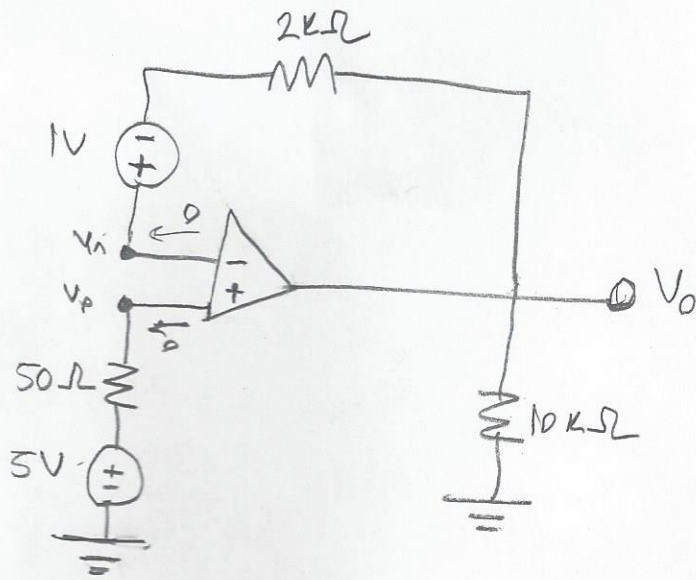


①



$$V_O = ?$$

$$V_P = 5V$$

$$V_N = 5V$$

$$V_O = 4V$$