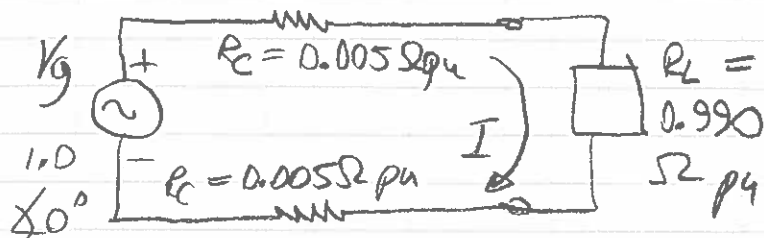


Case Study - 1 ϕ , 3 ϕ , & others, Cu required C Abraham 18 Mar 2016 1/2




$$I = \frac{V_g}{2R_c + R_L} = \frac{1.00 \text{ A pu } \angle 0^\circ}{2(0.005) + 0.990}$$

$$P_L = I^2 R_L = (1.00 \text{ A})^2 (0.990 \Omega) = 0.990 \text{ W pu}$$

$$P_c = 2I^2 R_c = 2(1.00 \text{ A})^2 (0.005 \Omega) = 0.010 \text{ W pu}$$

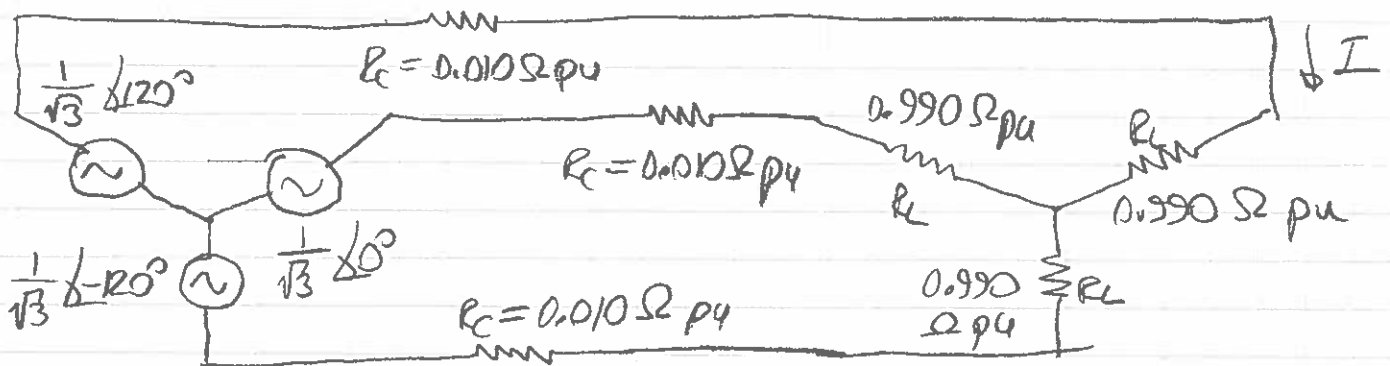So we wish to transmit the same 0.990 W pu to load, losing only 0.010 W in cables, over same distance. Line-to-neutral voltage must be $\frac{1}{\sqrt{3}}$ since line-to-line must equal 1.0, for same insulation.



$$I \text{ (per phase)} = \frac{V_{L-N}}{R_c + R_L} = \frac{(1/\sqrt{3}) \text{ V}}{(0.010 + 0.990) \Omega} = \frac{1}{\sqrt{3}} \text{ A pu per phase}$$


$$P_L = I^2 R_L \text{ per phase} = \left(\frac{1}{\sqrt{3}} \text{ A}\right)^2 (0.990 \Omega) = 0.330 \text{ W pu/phase} \Rightarrow P_L = 0.990 \text{ W pu total, like } 1\phi \text{ case.}$$

$$P_c = I^2 R_c = \left(\frac{1}{\sqrt{3}} \text{ A}\right)^2 (0.010 \Omega) = 0.003333 \text{ W pu} \Rightarrow \text{total} = 0.010 \text{ W pu as was the case in } 1\phi.$$

Equal power lost in cables, equal power to load requires 50 mΩ cables in 1-phase, 10 mΩ cables in 3-phase. The 3-phase area can be half of 1-phase for 2X resistance, or 50%. But 3 ϕ has 3 cables, 1 ϕ has 2 cables; so 3-phase requires 75% the copper.

Case Study - 1 ϕ , 3 ϕ , & others, Cu required, C Abraham 18 Mar 2016 2/2

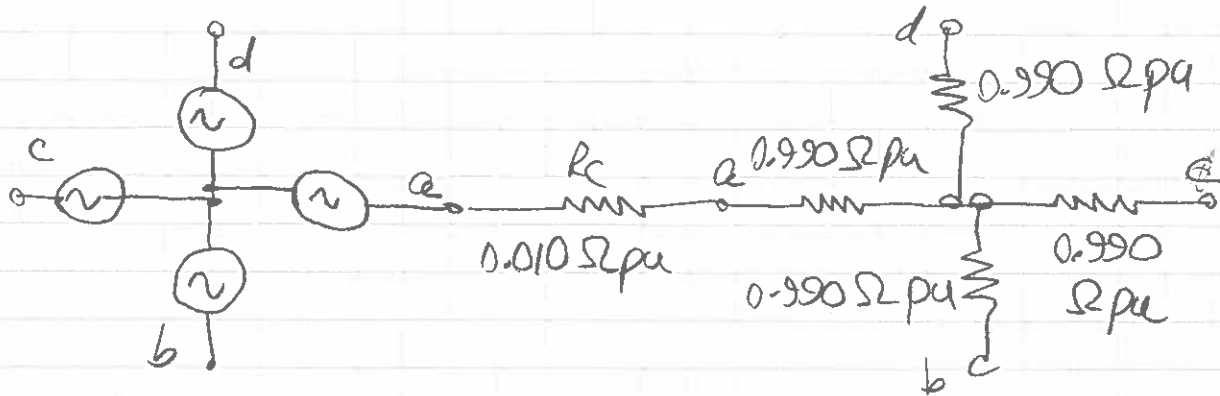For a 4-phase system, V_{L-N} must be 0.50 Vpu to keep V_{L-L} at 1.00 Vpu.



$$I(\text{per phase}) = \frac{V_{L-N}}{R_c + R_L} = \frac{(0.50 \text{ V})}{(0.990 + 0.010) \Omega} = 0.50 \text{ A pu per phase}$$

$$P_L = I^2 R_L = (0.50 \text{ A})^2 (0.990 \Omega) = 0.245 \text{ W pu per phase}$$

$$\Rightarrow \times 4 \text{ phases} \Rightarrow \underline{0.990 \text{ W pu}}, \text{ just as before.}$$

$$P_c (\text{per phase}) = I^2 R_c = (0.50 \text{ A})^2 (0.010 \Omega) = \underline{0.0025 \text{ W pu}}$$

$$\Rightarrow \times 4 \text{ phases} \Rightarrow \underline{0.010 \text{ W pu}}, \text{ just as before.}$$

Equal power is lost in cables & equal power delivered to load.

With 1-phase 5.0 m Ω cables are needed, $\times 2$ cables.

With 4-phase 10 m Ω cables are needed, $\times 4$ cables.

With 4-phase, we can allow cables with 2+times the resistance of 1-phase, so we only need half, or 50% of the copper per cable. But 4 cables vs. 2 cables means that 4-phase requires 100% the copper of 1-phase.

Claude

