

$V = 5$  volts  
 $I = 0.004$  amps  
 $R_1 = 100$  ohms  
 $R_2 = 200$  ohms  
 $R_3 = 350$  ohms

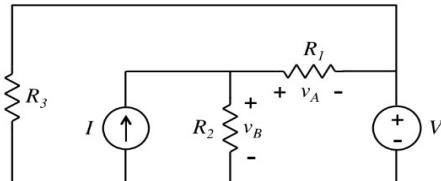


Figure 4-1

$$\begin{aligned}
 -I_V - I_{R1} + I_{R3} &= 0 \\
 I_V &= -I_{R1} + I_{R3} \\
 V_I &= 5.0 \text{ volts} \\
 I_V &= 0.028 \text{ amps} \\
 V_I &= V_1 \\
 V_I &= 3.6 \text{ volts} \\
 I &= 0.004 \text{ amps}
 \end{aligned}$$

$$\begin{aligned}
 V_{R1} &= V_1 - V_2 \\
 I_{R1} &= V_{R1} / R_1 \\
 V_{R1} &= -1.4 \text{ volts} \\
 I_{R1} &= -0.014 \text{ amps}
 \end{aligned}$$

$$\begin{aligned}
 V_{R2} &= V_1 \\
 I_{R2} &= V_1 / R_2 \\
 V_{R2} &= 3.6 \text{ volts} \\
 I_{R2} &= 0.018 \text{ amps} \\
 V_{R3} &= V_2 \\
 I_{R3} &= V_{R3} / R_3 \\
 V_{R3} &= 5.0 \text{ volts} \\
 I_{R3} &= 0.014 \text{ amps}
 \end{aligned}$$

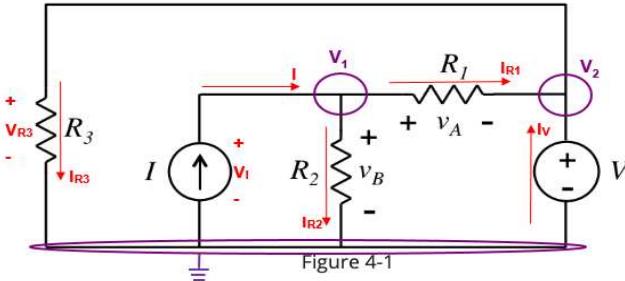


Figure 4-1

Node Voltage Method ( Kirchoff's Current Law ) :

KCL at Node 1 :

$$\begin{aligned}
 -I + V_1 / R_2 + (V_1 - V_2) / R_1 &= 0 \\
 V_1 / R_2 + (V_1 - V_2) / R_1 &= I \\
 R_1 V_1 + R_2 (V_1 - V_2) &= I R_1 R_2 \\
 R_1 V_1 + R_2 V_1 - R_2 V_2 &= I R_1 R_2 \\
 (R_1 + R_2) V_1 - R_2 V_2 &= I R_1 R_2 \\
 300 V_1 + -200 V_2 &= 80
 \end{aligned}$$

KCL at Node 2 : not necessary because  $V_2 = V$

$$0 V_1 + 1 V_2 = 5$$

Power Table				
Device	Voltage (volts)	Current (amps)	Power Delivered (watts)	Power Absorbed (watts)
V	5.0	0.028	0.1414	
I	3.6	0.004	0.0144	
R <sub>1</sub>	-1.4	-0.014		0.0196
R <sub>2</sub>	3.6	0.018		0.0648
R <sub>3</sub>	5.0	0.014		0.0714
TOTAL			0.1558	0.1558

Solving 2 equations with 2 unknowns:

	K1	K2	Constant
Eq. 1	300	-200	80
Eq. 2	0	1	5

Variable

$V_1 =$	3.6
$V_2 =$	5.0