

Obtain v_o in the circuit of Fig. 3.54.

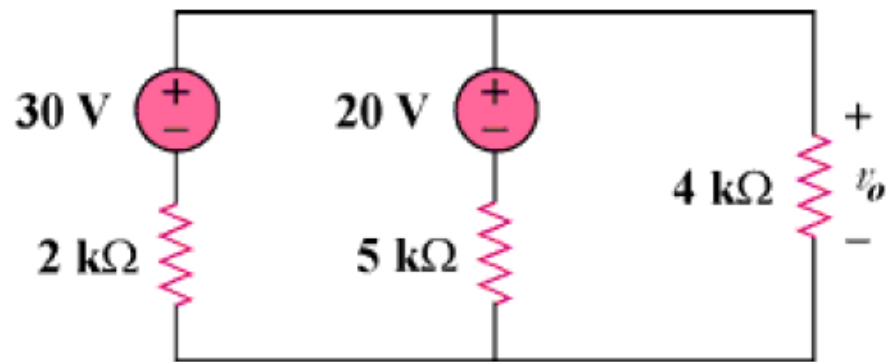


Figure 3.54