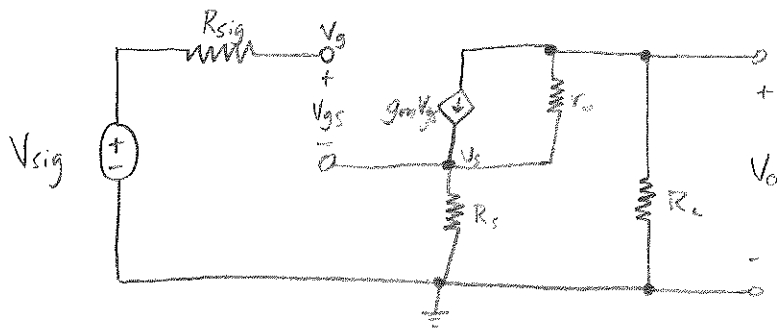


1.



$$\textcircled{1} \frac{V_o - 0}{R_L} = g_m V_{gs} + \frac{V_o - V_s}{r_o}$$

$$\textcircled{2} \begin{aligned} V_{gs} &= V_g - V_s \\ &= V_{sig} - V_s \end{aligned}$$

$$\textcircled{3} \frac{V_s - 0}{R_s} = \left(-\frac{V_o}{R_L} \right) R_s$$

$$V_s = -\frac{V_o R_s}{R_L}$$

$$\textcircled{2} \rightarrow \textcircled{1}: \frac{V_o}{R_L} = g_m (V_{sig} - V_s) + \frac{V_o - V_s}{r_o}$$

$$\frac{V_o}{R_L} = g_m V_{sig} - g_m V_s + \frac{V_o - V_s}{r_o}$$

$$\text{Now Plug } \textcircled{3} \text{ in: } \frac{V_o}{R_L} = g_m V_{sig} - g_m \left(-\frac{V_o R_s}{R_L} \right) + \frac{V_o + \frac{V_o R_s}{R_L}}{r_o}$$