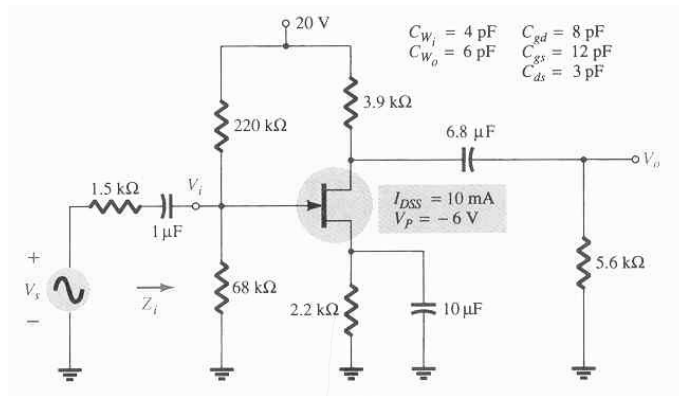


1.




- Determine V_{GSQ} and I_{DQ} .
- Find g_{m0} and g_m .
- Calculate the midband gain of $A_v = V_o/V_i$.
- Determine Z_i .
- Calculate $A_{vs} = V_o/V_s$.
- Determine f_{LG} , f_{LC} and f_{LS} for the capacitors $1\mu F$, $6.8\mu F$ and $10\mu F$, respectively.
- Determine the low-cutoff

frequency.


- Sketch the low-frequency response for the amplifier using the results of part (f).
- Determine f_{Hi} and f_{Ho} .
- Determine the high-cutoff frequency.
- Sketch the frequency response for the high-frequency region using the results of part (i).

2.

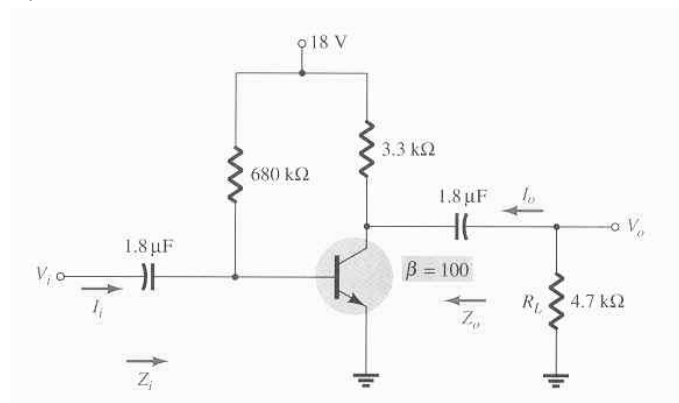


- Determine A_{vNL} , Z_i and Z_o .
- Calculate the gain A_{vL} .
- Determine the current gain A_{iL} .
- Determine A_{vL} , A_{iL} , Z_i and Z_o using the r_e model.

3.

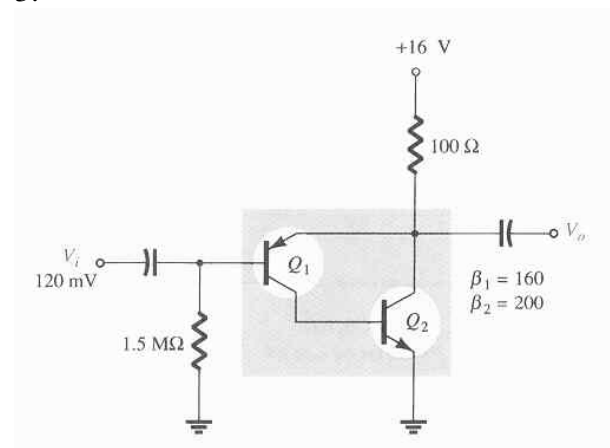


- Calculate the dc bias values of V_{B1} , V_{C2} and I_C .
- Calculate the output ac voltage.

4.

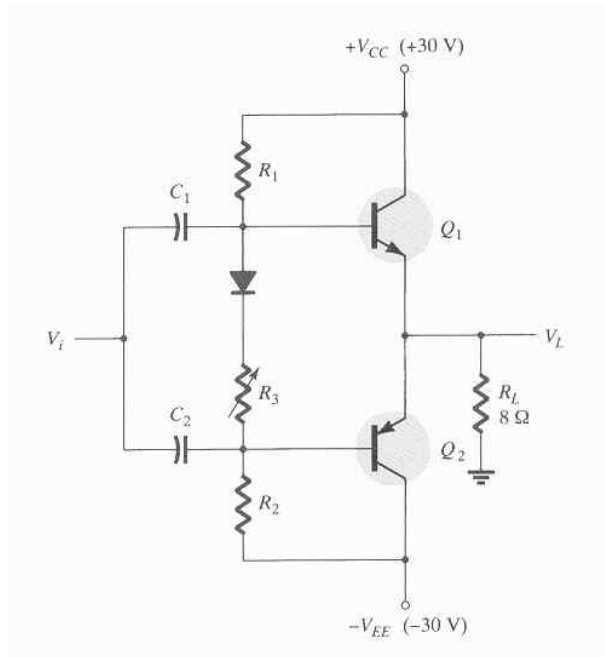

- $P_i(dc)$.
- $P_o(ac)$
- $\% \eta$
- Power dissipated by both power output transistors.

5.

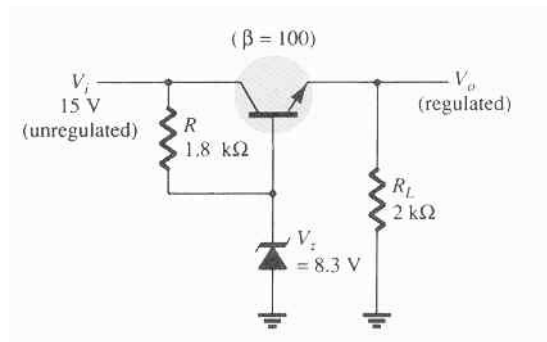

Calculate the output voltage and Zener diode current in the regulator circuit.