

$$(a) I_1 = \frac{V^+ - V^- - 2V_{BE}}{R_1} = \frac{30 - 1.4}{28.6} = 1 \text{ mA}$$

$$I_{C3} = I_1 = \boxed{1 \text{ mA}}$$

$$I_{C1} = I_{C2} = \frac{I_1}{2} = \boxed{0.5 \text{ mA}}$$

$$V_{O2} = V^+ - I_{C2} R_C = 15 - 0.5(20) = 5 \text{ Volts}$$

$$I_{C6} = \frac{V^+ - V_{O2} - V_{BE}}{6} = \frac{15 - 5.7}{6} = \boxed{1.55 \text{ mA}}$$

$$(b) r_{\pi 1} = \frac{V_T \beta}{I_{C1}} = \frac{0.026(100)}{0.5} = 5.2 \text{ k}\Omega$$

$$r_{\pi 6} = \frac{\beta V_T}{I_{C6}} = \frac{0.026(100)}{1.55} = 1.67 \text{ k}\Omega$$

$$R_{i66} = r_{\pi 6} + (1 + \beta) R_E = 1.67 + 101(4.3) = 435.97$$

$$\frac{V_{O2}}{V_d} = \frac{\beta (R_d \parallel R_{i66})}{2(r_{\pi 1} + R_d)} = \frac{100(19.122)}{2(5.2 + 2)} = \boxed{132.8}$$

$$(c) R_o = \frac{V_A}{I_{C3}} = \frac{80}{1} = 80 \text{ k}\Omega$$

Yes,  $A_v = \frac{\text{something}}{\text{something}(R_o)}$  so if  $R_o$  changes so will  $A_v$ .

(d) This i'm not sure about but here is an attempt  
 $A_d = A_{d1} \neq A_2$  where  $A_2 = 1$

$$\text{so } \boxed{A_d = A_{d1} = 132.8}$$