

4-9 TABLE OF CONDUCTIVITIES

The conductivities σ (for direct current) of some common materials are listed in Table 4-1 for a temperature of 20°C and for a superconductor at temperatures below 21 K. See page 123.

4-10 KIRCHHOFF'S VOLTAGE LAW AND THE DIFFERENCE BETWEEN POTENTIAL AND EMF

Consider the simple electric circuit shown by the schematic diagram in Fig. 4-9. The circuit consists of a resistor R_0 and the battery. The current is I at all points in the circuit. At any point in the conducting material of the circuit we have from Ohm's law at a point that $\mathbf{J}/\sigma = \mathbf{E}$, where \mathbf{E} is the total field at the point.

In general the total field \mathbf{E} may be due not only to static charges but also to other causes such as the chemical action in a battery. To indicate this explicitly, we write

$$\mathbf{E} = \mathbf{E}_c + \mathbf{E}_e \quad (1)$$

where \mathbf{E}_c = static electric field due to charges; the subscript c indicates explicitly that the field is due to *charges*

\mathbf{E}_e = electric field generated by other causes as by a battery; the subscript e indicates explicitly that it is an *emf-producing* field

Whereas \mathbf{E}_c is derivable as the gradient of a scalar potential due to charges ($\mathbf{E}_c = -\nabla V$), this is not the case for \mathbf{E}_e . Substituting (1) in (4-7-2), writing $\mathbf{J} = I/a$, where a is the cross-sectional area of the conductor, and noting the value of σ from (4-6-2), we have

$$\frac{\mathbf{J}}{\sigma} = \mathbf{I} \frac{R}{l} = \mathbf{E}_c + \mathbf{E}_e \quad (2)$$

where R/l is the resistance per unit length in ohms per meter. This applies at any point in the circuit. Integrating around the complete circuit gives

$$\oint \mathbf{E}_c \cdot d\mathbf{l} + \oint \mathbf{E}_e \cdot d\mathbf{l} = I \oint \frac{R}{l} dl \quad (3)$$

The first term is zero; i.e., the line integral of a field due to charges is zero around a closed circuit (see Sec. 2-8, last paragraph). However, the second term involving the line integral of \mathbf{E}_e around the circuit is not zero but is equal to a voltage called

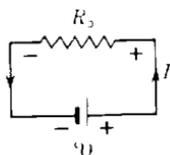


Figure 4-9 Series circuit of battery and external resistance.