

---

# CHALLENGE YOURSELF

- 3** A  $2\ \mu\text{F}$  capacitor is charged by connecting to a  $12\ \text{V}$  battery. The battery is disconnected and the capacitor is connected to an uncharged  $4\ \mu\text{F}$  capacitor. Calculate the change in energy stored.
-