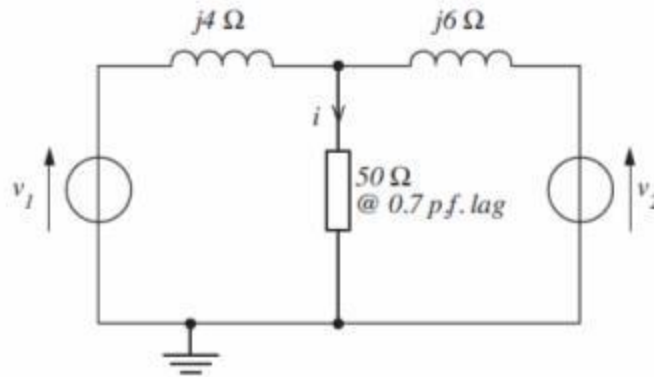


The diagram below shows a $50\ \Omega$ load being fed from two voltage sources via their associated reactances. Determine the current i flowing in the load by using:

- Thevenin's theorem
- The superposition theorem




$$v_1 = \sqrt{2} \times 415 \cos(100\pi t) \text{ volts}$$

$$v_2 = \sqrt{2} \times 415 \sin(100\pi t) \text{ volts}$$

Solution:

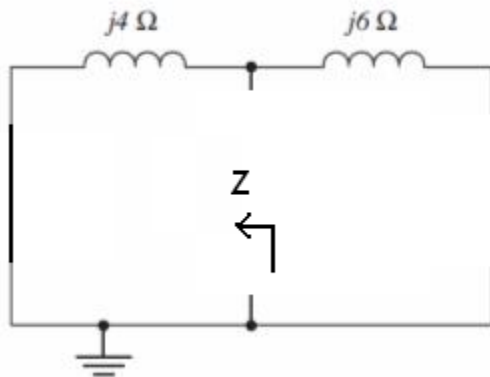- Using Thevenin's Theorem, we'll read the impedance from the load side and turn off the voltage sources by replacing them with a shorted wire:




The equivalent impedance is:

$$Z = \frac{(j4)(j6)}{j4 + j6}$$

$$Z = \frac{-24 \left(\frac{j}{j} \right)}{j10}$$

$$Z = j2.4\Omega$$

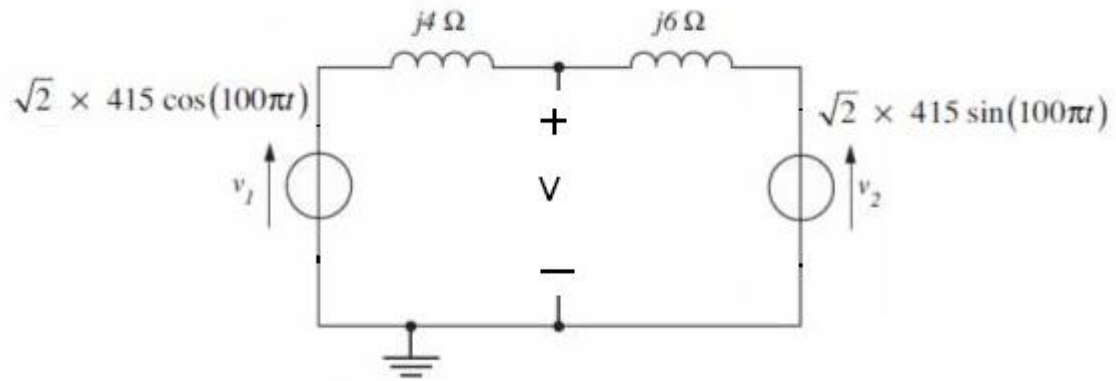Then we'll return the voltage sources and leave the load terminals open to read the voltage across the load:



Using nodal analysis, we have:

$$I_{L1} = I_{L2}$$

$$\frac{v_1 - v_L}{j4} = \frac{v_L - v_2}{j6}$$

$$\frac{415\sqrt{2} \cos(100\pi t) - v_L}{j4} = \frac{v_L - 415\sqrt{2} \sin(100\pi t)}{j6}$$

$$\frac{415\sqrt{2} \sin(100\pi t + 90) - v_L}{j4} = \frac{v_L - 415\sqrt{2} \sin(100\pi t)}{j6}$$

$$\frac{j415\sqrt{2} - v_L}{j4} = \frac{v_L - 415\sqrt{2}}{j6}$$

$$(j415\sqrt{2} - v_L)(j6) = (v_L - 415\sqrt{2})(j4)$$


$$-2490\sqrt{2} - j6v_L = j4v_L - j1660\sqrt{2}$$

$$-2490\sqrt{2} + j1660\sqrt{2} = j10v_L$$

$$v_L = 166\sqrt{2} + j249\sqrt{2}$$

$$v_L = 423.22 \sin(100\pi t + 56.31^\circ) \text{ Volts}$$

So the Thevenin model will be:

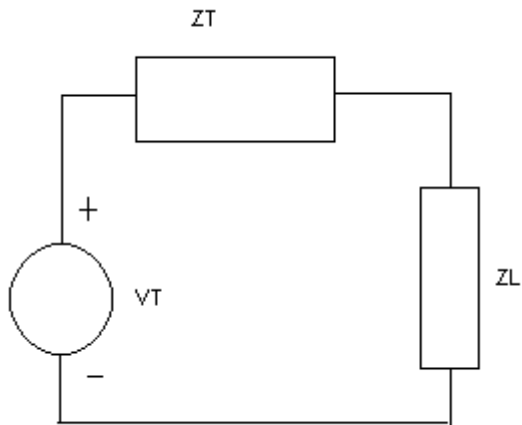

The equivalent load impedance is equal to:

$$R = 50\Omega$$

$$X = 50 \tan(\cos^{-1} 0.7) = 51.01\Omega$$

$$Z = R + jX = 50 + j51.01$$

Computing for the load current, we have:

$$Z_{EQ} = Z_T + Z_L$$

$$Z_{EQ} = Z_T + Z_L$$

$$Z_{EQ} = j2.4 + 50 + j51.01$$

$$Z_{EQ} = 50 + j53.41\Omega$$

$$I_L = \frac{V_T}{Z_{EQ}}$$


$$I_L = \frac{423.22 \sin(100\pi t + 56.31)}{50 + j53.41}$$

$$I_L = \frac{423.22 \angle 56.31}{73.16 \angle 46.89}$$

$$I_L = 5.78 \angle 9.42$$

$$I_L = 5.78 \sin(100\pi t + 9.42^\circ)A$$

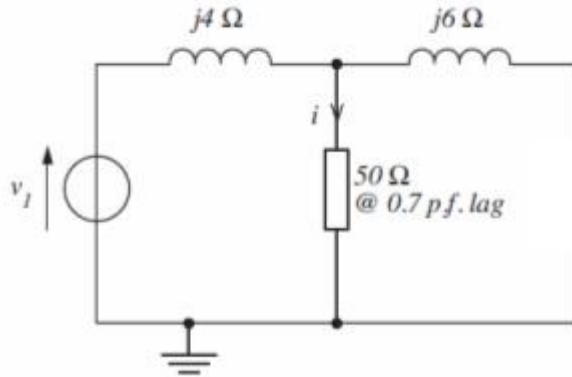- b. Using superposition, we first turn off one voltage and compute for the current with the other voltage turned on. So we have:



Solving, we have:

$$v_{L1} = (415\sqrt{2} \cos(100\pi)) \left(\frac{(50 + j51.01)(j6)}{50 + j51.01 + j6} \right) \left(j4 + \left[\frac{(50 + j51.01)(j6)}{50 + j51.01 + j6} \right] \right)$$

$$v_{L1} = (j415\sqrt{2}) \left(\frac{-306.06 + j300}{50 + j57.01} \right) \left(j4 + \left[\frac{-306.06 + j300}{50 + j57.01} \right] \right)$$

$$v_{L1} = (j415\sqrt{2}) \left(\frac{0.31 + j5.64}{j4 + 0.31 + j5.64} \right)$$

$$v_{L1} = (j415\sqrt{2}) \left(\frac{0.31 + j5.64}{0.31 + j9.64} \right)$$


$$v_{L1} = (j415\sqrt{2})(0.59 - j0.01)$$

$$v_{L1} = 5.87 + j346.27$$

$$I_{L1} = \frac{5.87 + j346.27}{50 + j51.01}$$

$$I_{L1} = 3.52 + j3.33A$$

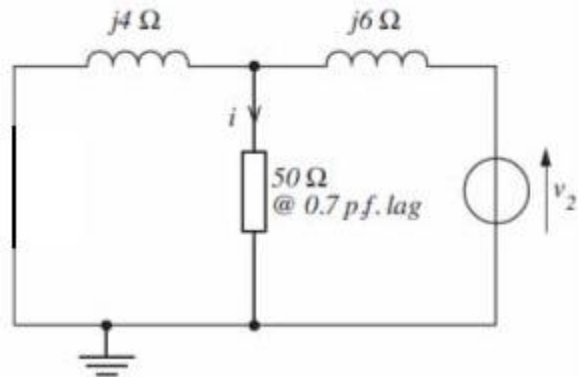We now turn on the other voltage and turn off the first one:



Solving, we have:

$$v_{L2} = (415\sqrt{2} \sin(100\pi)) \left(\frac{(50 + j51.01)(j4)}{50 + j51.01 + j4} \right) \left(j6 + \left[\frac{(50 + j51.01)(j4)}{50 + j51.01 + j4} \right] \right)$$

$$v_{L2} = (415\sqrt{2}) \left(\frac{-204.04 + j200}{50 + j55.01} \right) \left(j6 + \left[\frac{-204.04 + j200}{50 + j55.01} \right] \right)$$

$$v_{L2} = (415\sqrt{2}) \left(\frac{0.14 + j3.84}{j6 + 0.14 + j3.84} \right)$$

$$v_{L2} = (415\sqrt{2}) \left(\frac{0.14 + j3.84}{0.14 + j9.84} \right)$$

$$v_{L2} = (415\sqrt{2})(0.39 - j0.01)$$

$$v_{L2} = 228.89 - j5.87$$

$$I_{L2} = \frac{228.89 - j5.87}{50 + j51.01}$$

$$I_{L2} = 2.18 - j2.35A$$

Combining the solved current values, we have the final current value of:

$$I_L = 3.52 + j3.33 + (2.18 - j2.35)$$

$$I_L = 5.7 + j0.98$$

$$I_L = 5.78 \sin(100\pi + 9.76^\circ)A$$

Comparing both the Thevenin and the superposition solutions, both are relatively close answers.