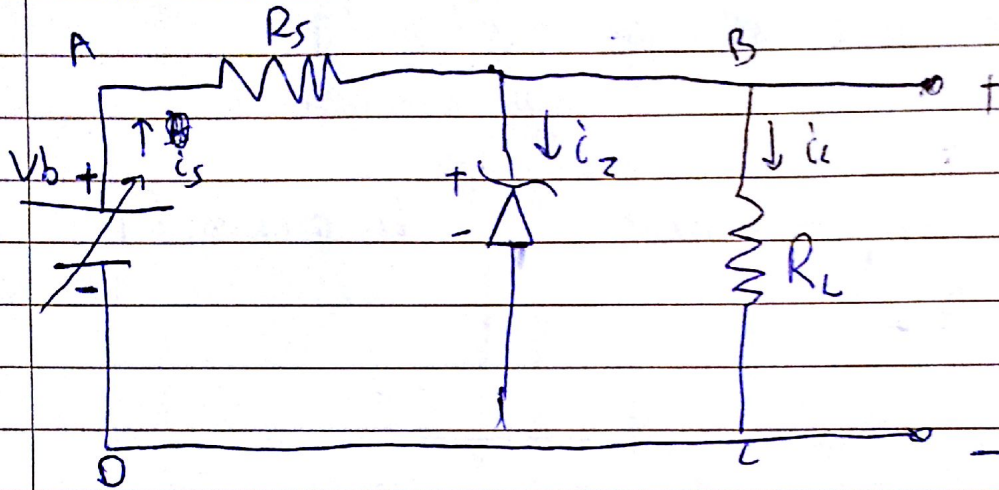


This diode zener has breakdown voltage equal to $V_z = 8.2V$ for currents: $75mA \leq i_z \leq 1A$. If $R_L = 9\Omega$, how much must R_s be, so that $V_L = V_z = 8.2V$, while V_b changes at about $\pm 10\%$ in relation with ~~the nominal~~ the nominal operating current displayed in the data sheet, which is $12V$?



1st question: In this exercise nothing is told about whether or not the zener diode is ideal. So in this case I assume that it is not ideal, or because it must be $V_L = V_z = 8.2$ I assume that it is ideal, due to the fact that if there were a ~~zener~~ zener resistance, then ~~V_L~~ $V_L > V_z$?

Solution

In order for the diode zener to maintain its voltage across it, a higher voltage must ~~be~~ ^{exist} across it, meaning that $V_{th} > V_z = 8.2V$

If I use the Thevenin theorem across the diode I get $V_{th} = \frac{R_L}{R_s + R_L} V_b$

$$\text{So } V_{th} > V_z \Rightarrow \frac{9}{R_s + 9} V_b > 8.2 \quad (1)$$

$$\bullet \quad i_s = i_z + i_L = i_z + \frac{V_L}{R_L} = i_z + 0,91$$

$$\Rightarrow \frac{V_b - V_z}{R_s} = i_z + 0,91 \Rightarrow \frac{V_b - V_z}{R_s} - 0,91 = i_z$$

$$\text{So } 0,075 \leq \frac{V_b - V_z}{R_s} - 0,91 \leq 1 \quad (\Rightarrow)$$

$$\frac{0,485}{R_s} \leq \frac{V_b - 8,2}{R_s} \leq 1,91 \quad (1)$$

For ~~Vb~~ Also $V_b \in [10,8, 13,2]$ because of the $\pm 10\%$

$$\text{So for } V_b = 10,8 \quad (2) \Rightarrow 1,3612 \leq R_s \leq 2,64$$

$$\text{For } V_b = 13,2 \quad (2) \Rightarrow 2,6178 \leq R_s \leq 5,076$$

So in order to have the whole range of $V_b \Rightarrow 1,3612 \leq R_s \leq 5,076$

$$\bullet \text{ But } \frac{9}{R_s + 9} V_b > 8,2 \Rightarrow$$

$$\text{If } V_b = 10,8 \text{ V } \Rightarrow R_s < 2,88$$

$$V_b = 13,2 \text{ V } \quad R_s < 5,48$$

So in order to have the whole range $R_s < 2,88$

Finally in order to have:

$$\bullet \quad 0,075 \leq i_z \leq 1$$

$$\bullet \quad V_z = V_L = 8,2 \text{ V}$$

$$\bullet \quad V_{th} > V_z$$

$$\underline{R_s \in [1,3612, 5,48]}$$