

2. Determine, using the values given in TABLE A, the current  $I$  in the circuit of FIGURE 2 by:

(a) mesh analysis - I ALREADY KNOW THE ANSWER IS  $-9.2 + j17.30$  A

(b) nodal analysis. - I NEED TO FIND THE SAME ANSWER AS ABOVE USING NODAL ANALYSIS.

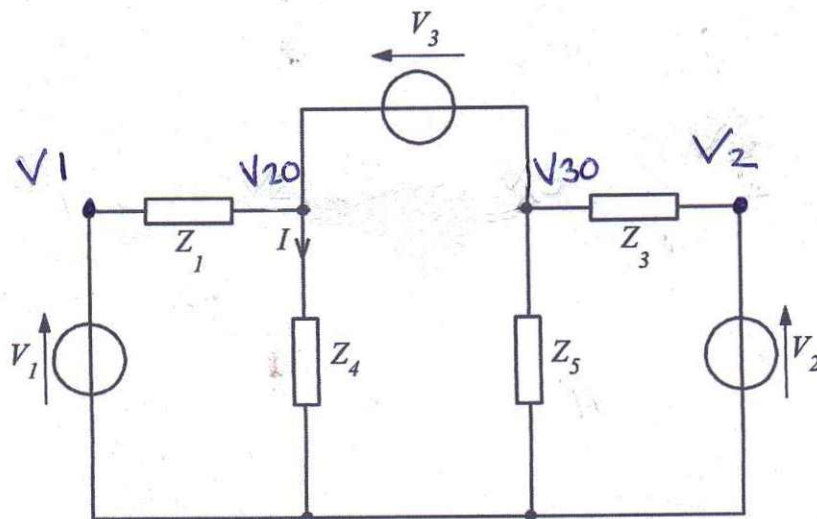


TABLE A

$V_1$	$120 \angle 0^\circ$ V
$V_2$	$120 \angle 0^\circ$ V
$V_3$	$20 \angle 45^\circ$ V
$Z_1$	$2 \Omega$
$Z_3$	$4 \Omega$
$Z_4$	$-j5 \Omega$
$Z_5$	$j4 \Omega$

THIS CIRCUIT IS THE SAME AS THE EXAMPLE I ATTACHED ON PAGE ① (FIG. 14) BUT WITHOUT THE PARALLEL RESISTANCE ACROSS  $V_3$ .

$$\frac{V_1 - V_{20}}{Z_1} - \frac{V_{20}}{Z_4} - \frac{V_{30}}{Z_5} + \frac{V_2 - V_{30}}{Z_3} = 0$$

$$\frac{120 - V_{20}}{2 \Omega} - \frac{V_{20}}{-j5 \Omega} - \frac{V_{30}}{j4 \Omega} + \frac{j120 - V_{30}}{4} = 0$$

I NEED TO SIMPLIFY  $-j5$  AND  $j4$ . I WILL DIVIDE THEM BY 1

$$\frac{120 - V_{20}}{2 \Omega} - (j0.2 V_{20}) + (j0.25 V_{30}) + \frac{j120 - V_{30}}{4 \Omega} = 0$$

I WILL MULTIPLY  $120(V_1) \times 4$  AND  $j120(V_2) \times 2$ . LCM IS 4

$$480 - 2V_{20} - (j0.2 V_{20}) + (j0.25 V_{30}) + j240 - V_{30} = 0$$