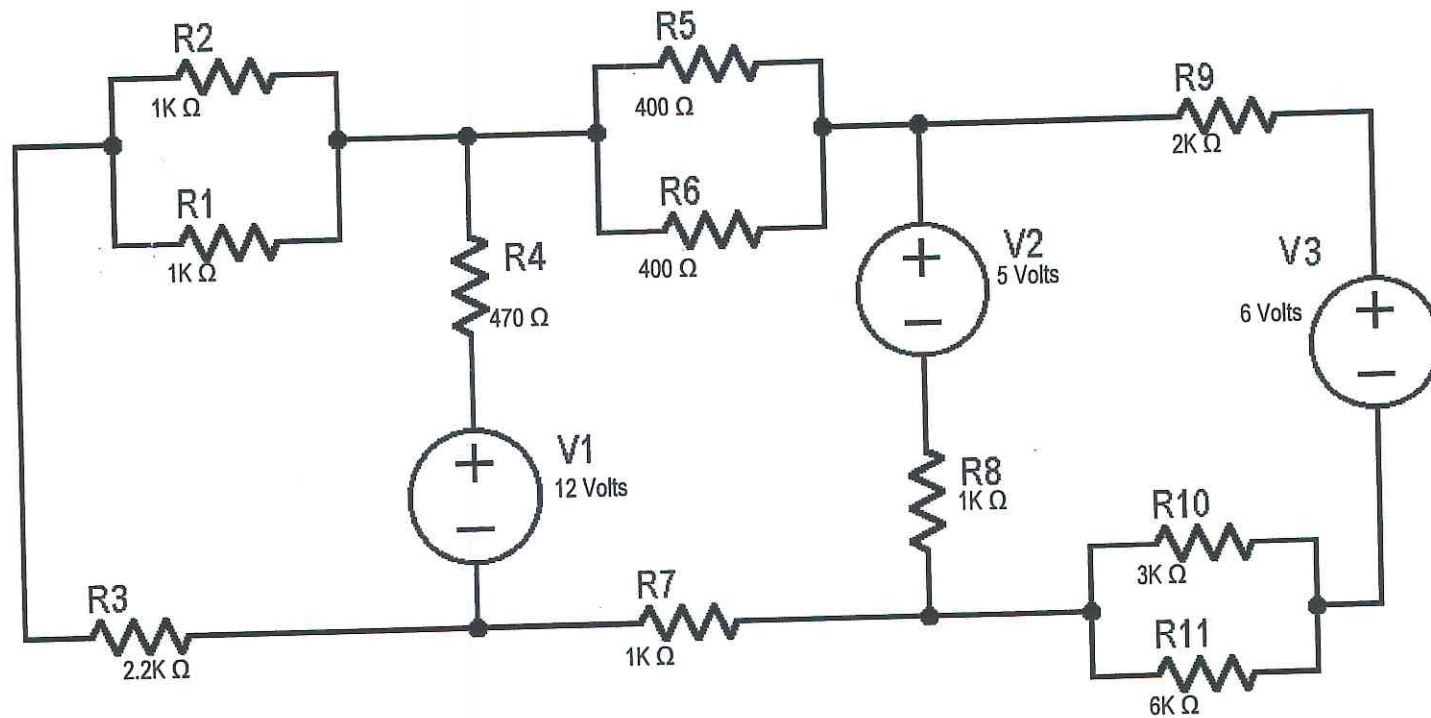


### Circuit Diagram:

Question: Find the current through resistor **R9**, and Voltage across the same resistor



Question ID: EEP 405

Qstn:

- Using **superposition Theorem**
- Calculate the voltage, current & power through the mentioned resistor.
- Test & Simulation results by using superposition theorem by using ECAD tool.