

$$5/a) \text{ Voltage regulation} = \frac{V_{RATING}}{V_1^2} (R'_p \cos \phi + X'_p \sin \phi) \times 100 \%$$

$$\text{Voltage regulation} = \frac{200 \times 10^3}{415^2} \times (0.014 \times 0.8 + 0.057 \times \sqrt{1 - 0.8^2}) \times 100 \% = 5.272 \%$$

$$b) \text{ Voltage regulation} = \frac{V_{RATING}}{V_1^2} R'_p \times 100 \%$$

$$\text{Voltage regulation} = \frac{200 \times 10^3}{415^2} \times 10 \times 10^{-3} \times 100 \% = 1.16 \%$$

$$I_1 = \frac{200 \times 10^3}{415} = 481.93 \text{ A} \quad I_2 = \frac{200 \times 10^3}{11 \times 10^3} = 18181818.18 \text{ A}$$