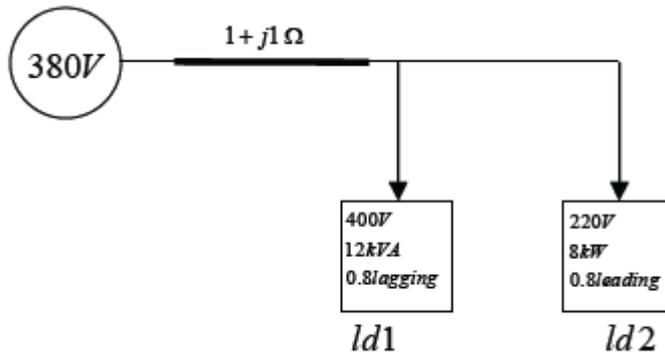


Question - A Three-phase circuit

A three-phase generator, with a combined (interlaced) voltage of 380 V is connected to two three-phased loads through a transmission line. The transmission line's impedance is $1 + j1 \Omega$. Both Loads are connected in parallel, and given in the values specified in the following scheme:



Calculate the current through the transmission line (magnitude and phase).

Attempt at a solution

Well, Basically the problem is that I get two different answers in two different ways:

First, I tried to calculate both currents flowing through both loads:

$$I_1 = \frac{S_1}{V_1} = \frac{12 \cdot 10^3}{400} = 30 \text{ A}$$

$$\cos(\phi_2) = \frac{P_2}{S_2} = 0.8 \Rightarrow S_2 = \frac{P_2}{0.8} = 10 \text{ kVA}$$

$$I_2 = \frac{S_2}{V_2} = \frac{10 \cdot 10^3}{220} = 45.45 \text{ A}$$

$$I = I_1 + I_2 = 30 + 45.45 = \boxed{75.45 \text{ A}}$$

For now, I am only focused on the magnitude.

Second way, is to simply calculate the equivalent load's Impedance using the information given, and then calculate the current:

$$Z_1 = \frac{V_1^2}{S_1} \angle \cos^{-1}(\phi_1) = \frac{400^2}{12 \cdot 10^3} \angle \cos^{-1}(0.8) = 13.33 \angle 36.87^\circ$$

$$Z_2 = \frac{V_2^2 \cos(\phi_2)}{P_2} \angle \cos^{-1}(\phi_2) = \frac{220^2 \cdot 0.8}{8 \cdot 10^3} \angle -\cos^{-1}(0.8) = 4.84 \angle -36.87^\circ$$

$$Z_{eq} = \frac{Z_1 Z_2}{Z_1 + Z_2} = 4.19 \angle -19.31^\circ$$

$$I_T = \frac{V}{Z_{eq} + (1 + j)} = \frac{380}{(4.19 \angle -19.31^\circ) + (1 + j)} = \boxed{76.47 \angle 4.45^\circ}$$

So the question is why I have some slight differences between both of the results I got (Magnitude only).