
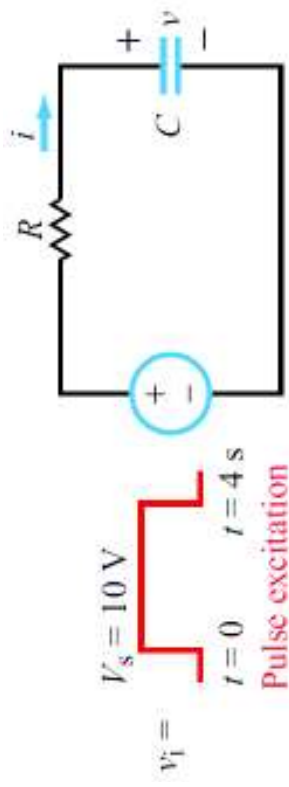



## Example: Rectangular Pulse

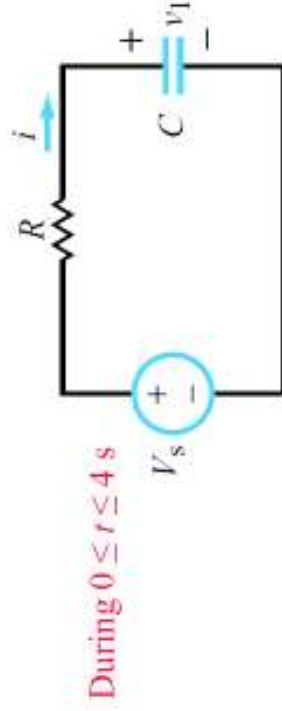

(a)



(b)

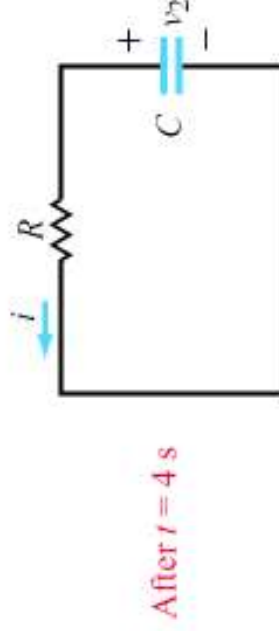

(c)

$$v_1(t) = V_s u(t) - V_s u(t - 4).$$

Since the circuit is linear, we can apply the superposition theorem to determine the capacitor response  $v(t)$ . Thus,

$$v(t) = v_1(t) + v_2(t),$$

$$\begin{aligned} v_1(t) &= v_1(\infty) + [v_1(0) - v_1(\infty)]e^{-t/\tau} \\ &= V_s(1 - e^{-t/\tau}) \quad (\text{for } t \geq 0). \end{aligned}$$

For  $V_s = 10 \text{ V}$  and  $\tau = RC = 25 \times 10^3 \times 0.2 \times 10^{-3} = 5 \text{ s}$ ,

$$v_1(t) = 10(1 - e^{-0.2t}) \text{ V} \quad (\text{for } t \geq 0).$$

The second step function has an amplitude of  $-V_s$  and is delayed in time by 4 s. Upon reversing the polarity of  $V_s$  and replacing  $t$  with  $(t - 4)$ , we have

$$v_2(t) = -10[1 - e^{-0.2(t-4)}] \text{ V} \quad (\text{for } t \geq 4 \text{ s}).$$

The total response for  $t \geq 0$  therefore is given by

$$\begin{aligned} v(t) &= v_1(t) + v_2(t) \\ &= 10[1 - e^{-0.2t}] - 10[1 - e^{-0.2(t-4)}] u(t - 4) \text{ V} \end{aligned}$$

