



Remote Control Car
This circuit controls two motors by 2 PWM and 2 Drivers
The direction is controlled by simple Relays