

3. For the balanced three-phase loads shown in FIGURE 3, $Z_Y = (15 + j15) \Omega$ and $Z_\Delta = (45 + j45) \Omega$. Determine:

- (a) the equivalent single Δ -connected load,
 (b) the equivalent single Y-connected load obtained from the Δ -Y transformation of (a) above,
 (c) the equivalent single Y-connected load obtained by transforming the Δ sub-load of FIGURE 3 to a Y and with the star-points of the two Y-sub-circuits connected together,
 (d) the total power consumed in case (a) above if the line voltage of the three-phase supply is 415 V at 50 Hz.

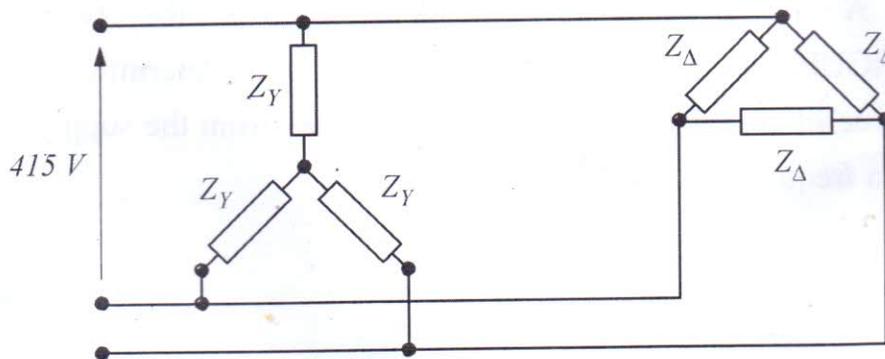


FIG. 3