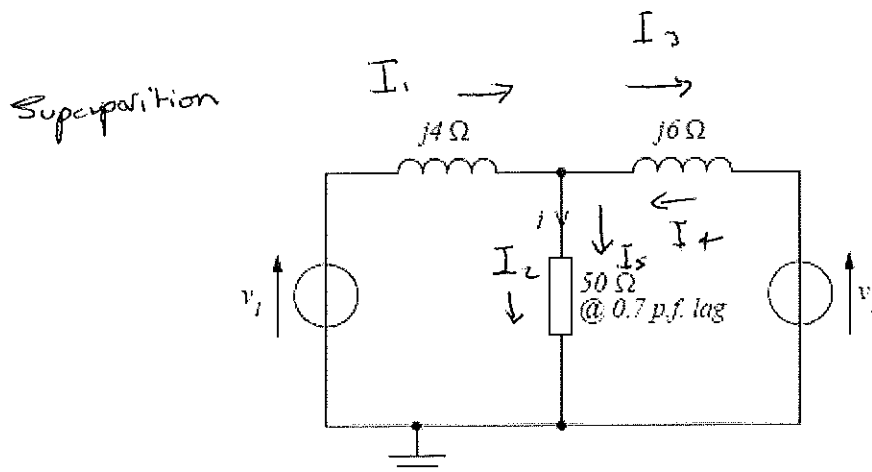


1. FIGURE 1 shows a $50\ \Omega$ load being fed from two voltage sources via their associated reactances. Determine the current i flowing in the load by:
- applying Thévenin's theorem
 - applying the superposition theorem
 - by transforming the two voltage sources and their associated reactances into current sources (and thus form a pair of Norton generators).



$$v_1 = \sqrt{2} \times 415 \cos(100\pi t) \quad \text{volts}$$

$$v_2 = \sqrt{2} \times 415 \sin(100\pi t) \quad \text{volts}$$

FIG. 1

16)

Removing V_z

Resistance $Z =$

$$I_4 + \frac{(35 + I_{35.71}) \times I_6}{35 + I_{35.71} + I_6}$$

$$= \frac{I_{210} - 214.26}{35 + I_{41.71}} + I_4$$

$$(I_{210} - 214.26) \times (35 - I_{41.71}) =$$

$$I_{350} + 8759.1 - 7499.1 + I_{8936.7846}$$

$$= I_{9286.78 \text{ to 2.d.p.}} + 1260$$

$$(35 + I_{41.71}) \times (35 - I_{41.71})$$

$$= 1225 + 1739.7241$$

So

$$\frac{I_{9286.78} + 1260}{2964.7241}$$

=

$$I_{3.132 \text{ to 3.d.p.}} + 0.4249 \text{ or } 0.425 \text{ to 3.d.p.}$$

2
Z total

$$Z = 17.132 + 0.425$$

$$I_1 = \frac{V}{Z}$$

$$\underline{1415}$$

$$17.132 + 0.425$$

$$= \underline{1176.375 + 2959.78}$$

$$\cancel{0.180} \quad 0.181 \text{ to } 3.d.p + 50.865421$$

$$= \underline{1176.375 + 2959.78}$$
$$51.046 \text{ to } 3.d.p$$

$$13.455 + 59.14119011 = I_1$$

$$I_2 = \left(\frac{I_6}{35 + 141.71} \right) I_1$$

$$I_6 (35 - 141.71) = 1210 + 250.26$$

$$(35 + 141.71) \times (35 - 141.71)$$

$$= 1225 + 1739.7241$$

$$= 2964.7241$$

$$\frac{I_{210} + 250.26}{2964.7241} = I_{0.71 \text{ to } 2.1} + 0.84 \text{ to } 2.1$$

So

$$(I_{3.455} + 59.141 \text{ to } 2.1) (I_{0.71} + 0.84) = I_z$$

$$- 2.45 \text{ to } 2.1 + I_{41.99 \text{ to } 2.1}$$

$$+ 49.67844 + I_{2.90 \text{ to } 2.1}$$

$$I_z = 47.2284 + I_{44.89}$$

Removing V_1

$$Z = \frac{I_4(35 + I_{35.71})}{I_4 + I_{35.71} + 35} + I_6$$

So

$$\frac{I_{140} - 142.84}{I_{39.71} + 35} + I_6$$

Removing (V.)

$$V_2 = 415 + I_0$$

parallel =

①

$$\frac{I_4 (35 + I_{35.71})}{I_4 + 35 + I_{35.7}}$$

$$I_4 + 35 + I_{35.7}$$

②

$$\frac{I_{140} - 142.84}{35 + I_{39.7}}$$

③

$$(I_{140} - 142.84) \times (35 - I_{39.7})$$

$$= I_{4900} - 4999.4 + 5558 + I_{5670.748}$$

So

$$I_{10570.748} + 558.6 \quad \text{Top}$$

$$(35 + I_{39.7}) \times (35 - I_{39.7})$$

$$1225 + 1576.09 = 2801.09 \quad \text{bottom}$$

$$\frac{I_{10570.748} + 558.6}{2801.09}$$

$$\text{Total resistance to } V_2 = I_{3.776} \text{ to } 2I_p + 0.2 \text{ to } 1I_p + I_6$$

$$= I_{9.77} + 0.2$$

$$\underline{470}$$

$$0.2 + J9.77$$

$$= 470 (0.2 - J9.77)$$

$$94 - J4591.9 = I_4$$

$$\text{So } I_s = \frac{I_4}{35 + J39.7} \times I_4$$

$$I_4 (35 - J39.7)$$

$$= J140 + 158.8 \quad T_{op}$$

$$1225 + 1576.09 = 2801.09$$

So

$$\frac{J140 + 158.8}{2801.09}$$

$$= J0.05 \text{ to } 2.d_p + 0.0567 \text{ to } 4.d_p$$

$$(94 - J4591.9) (J0.05 + 0.0567) = I_s$$

$$J4.7 + 229.595 + 5.3298 - J260$$

$$I_s = J255.7 \text{ to } 1.d_p + 234.923 \text{ to } 3.d_p$$