



- Find the current of the Norton equivalent generator and the Norton equivalent resistance.
- Find the voltage of the Thevenin generator and the Thevenin equivalent voltage.