
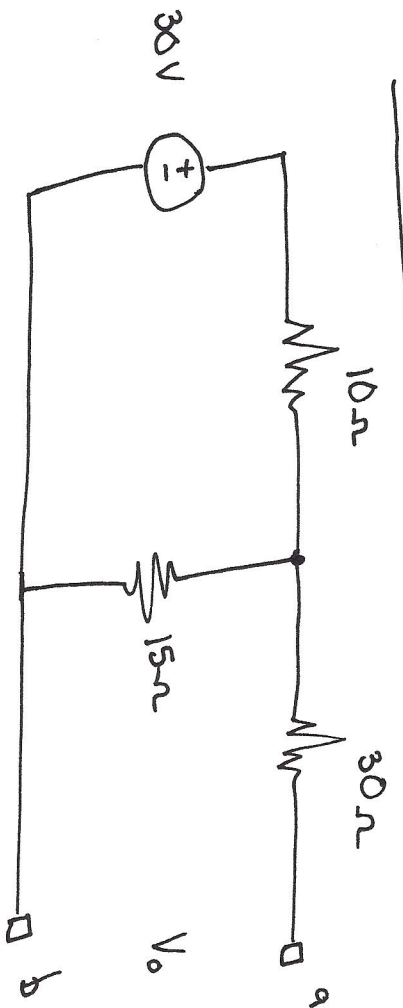


original

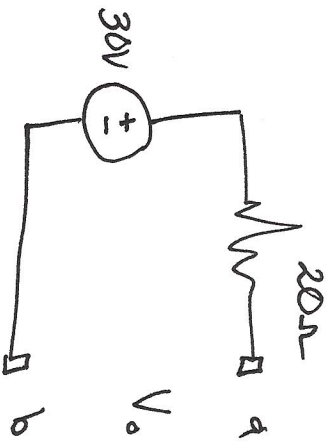

Redraw for open circuit  $V_o$ :



Redraw for  $I_{sc}$

