

Elec 275 – Principles of Electrical Engg
Quiz No.6 – Fall 2015

Name:

I.D.No:

6. In Fig 6,

- (a) Obtain the Thevenin Equivalent of the circuit connected to the load R_L
 (b) Obtain the value of R_L required for maximum power transfer and also find the value of the maximum power transferred, P_{max} (5 marks)

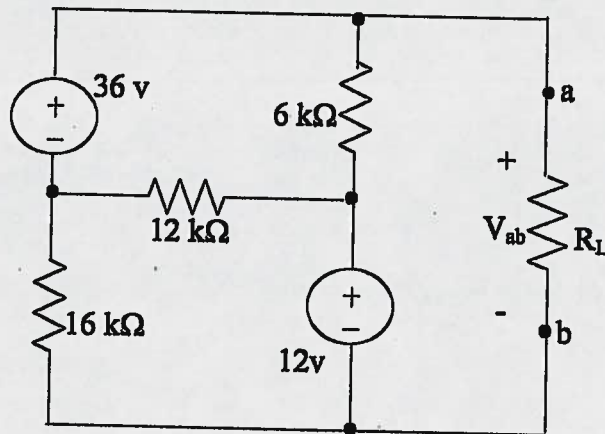


Fig.6.

Solution:

a) $V_{th} = V_{ab} = V_{oc}$ after removing R_L

$$KVL: 6I_1 + 12(I_1 - I_2) = 36$$


$$18I_1 - 12I_2 = 36$$

$$KVL: 12(I_2 - I_1) + 16I_2 = -12$$

$$-12I_1 + 28I_2 = -12$$


$$V_{ab} = 6I_1 + 12 = 6 \times 2.4 + 12 = 26.4 \text{ (V)} = V_{th}$$

To calculate R_{th} :

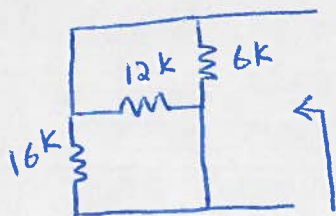


$$R_{th} \Rightarrow (6 \parallel 12 \parallel 16) = 3.2 \text{ k}\Omega$$

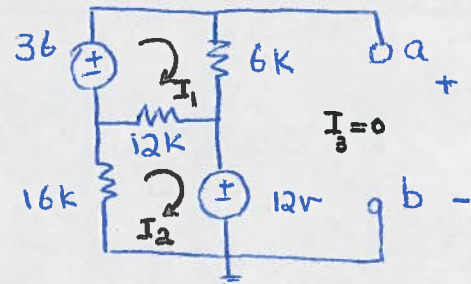b) MPT $\Rightarrow R_L = R_{th} = 3.2 \text{ k}\Omega$



$$I_1 = 2.4 \text{ (mA)}$$

$$I_2 = 0.6 \text{ (mA)}$$

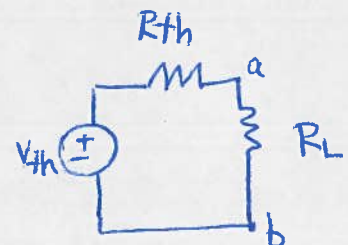

$$P_{Lmax} = \frac{V_{th}^2}{4 R_{th}} = 54.4 \text{ mW}$$