



Figure 2: R-L circuit.

(a) [2 marks]

Determine the transfer function of the circuit,  $T(\omega) = V_{\text{out}}(\omega)/V_{\text{in}}(\omega)$ , and express in the form  $A(\omega)e^{j\phi(\omega)}$ .

---