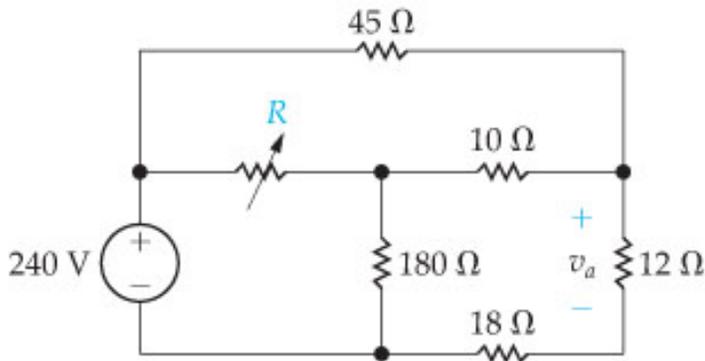


Problem 2.24

The variable resistor R is adjusted until $v_a = 60\text{V}$



Find the value of R

Express your answer to two significant figures and include the appropriate units.

Solution:

The current through the 12 Ohm resistor is $60\text{V}/12\text{ Ohm} = 5\text{A}$

The voltage across the 18 ohm resistor is therefore: $18\text{ Ohm} * 5\text{A} = 90\text{V}$

KVL around the large loop gives:

$$240\text{ V} - 45 * I (45\text{ ohm}) - 60 - 90 = 0$$

$$I (45\text{ ohm}) = 2\text{ A}$$

KCL at the node above the 12 ohm resistor now gives:

$$I (10\text{ ohm}) + I (45\text{ ohm}) = I (12\text{ ohm})$$

$$I (10\text{ ohm}) = 5\text{ A} - 2\text{ A} = 3\text{A}$$

The voltage drop going from left to right across the 10 ohm resistor is then:

$$V = IR = 3\text{A} * 10\text{ohm} = 30\text{V}$$

KVL around the rightmost loop gives the voltage across the 180 ohm resistor:

$$V (180\text{ Ohm}) - V (10\text{ohm}) - 60 - 90 = 0$$

$$V (180\text{ Ohm}) = 180\text{ V}$$

KCL gives the current through the variable resistor R :

$$I (\text{variable resistor}) = I (10\text{ ohm}) + I (180\text{ ohm}) = 3\text{ A} + 180/180 = 4\text{A}$$

Ohm's law gives the value of the variable resistor R :

$$(240\text{V} - 180\text{V}) = 4\text{A} * R$$

$$R = 15\text{ Ohm}$$